

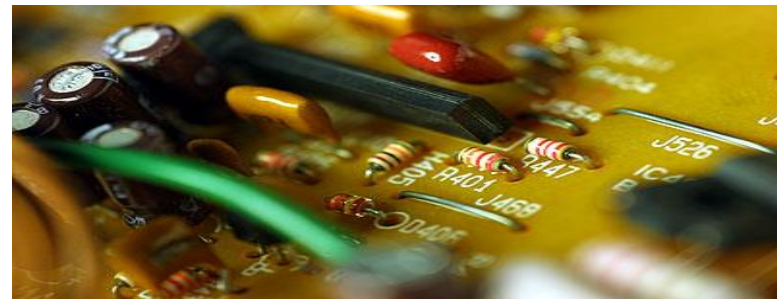


C02015

Basic Electronic Circuit Components

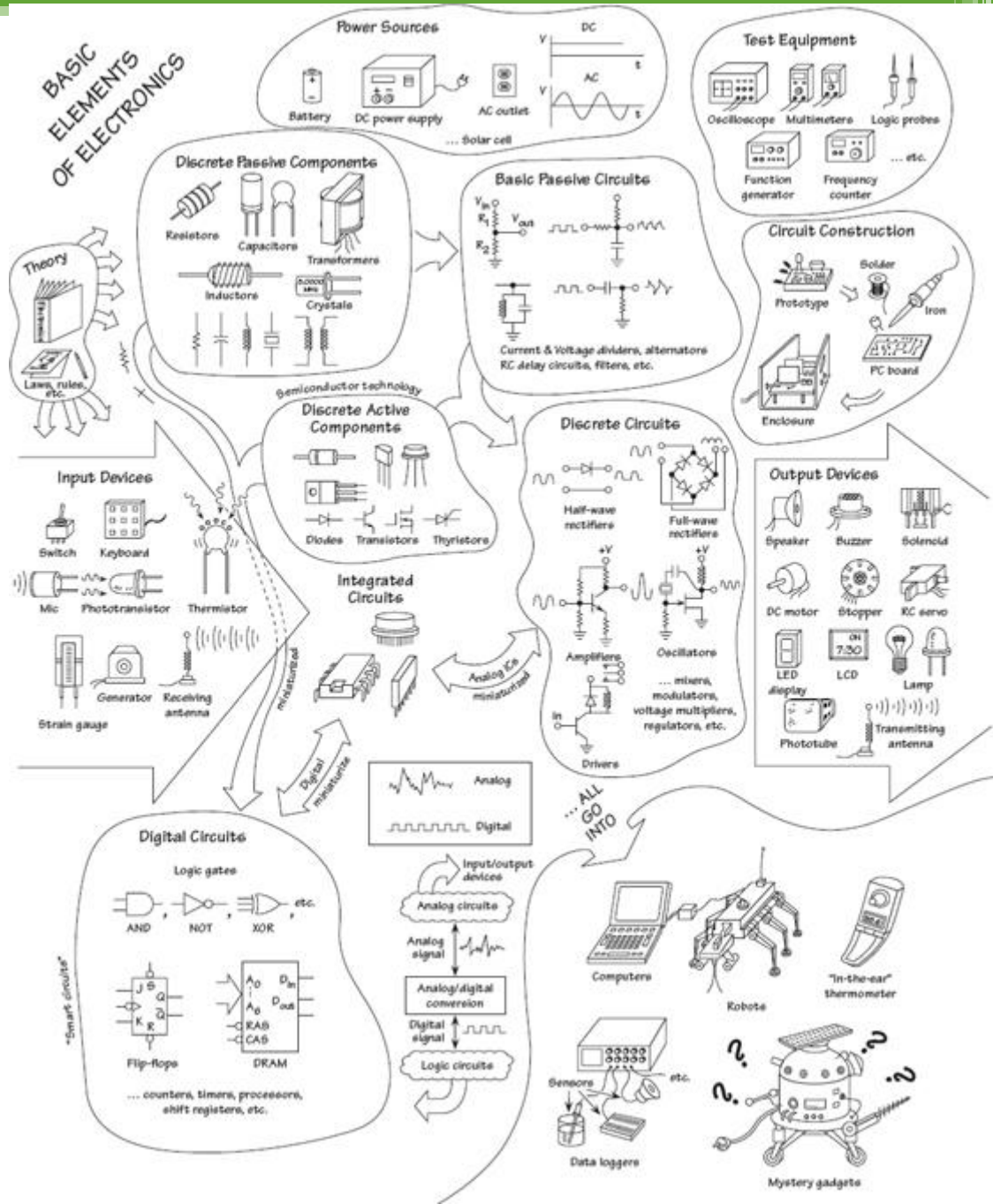

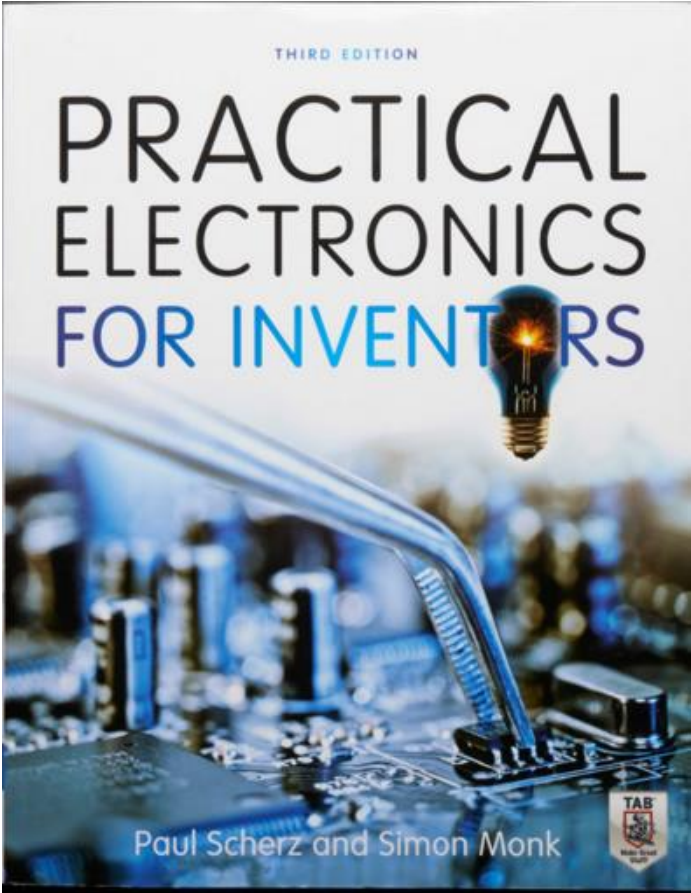




Actually....

- Circuit Analysis
- Electronics Components
 - Resistor, Capacitor, Transistor
- Hardware computer Exercise
 - Design and Layout the Circuit
- 20% for Midterm, 30% for Labs and 50% for final term
- Labs are very important (5 hour/ week)
 - *Don't share your report!!!!*

Some projects



Complicated Project

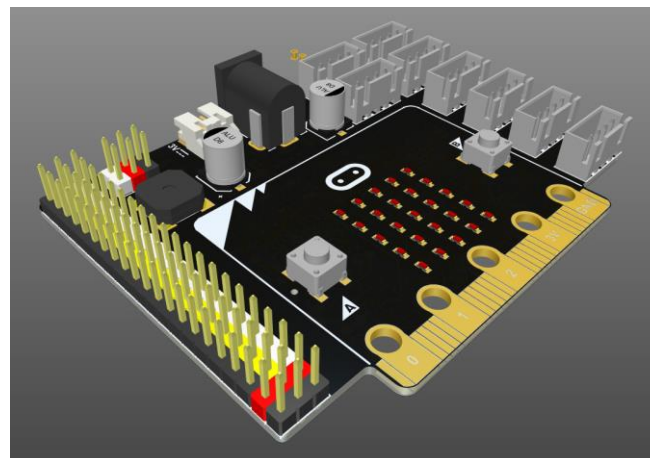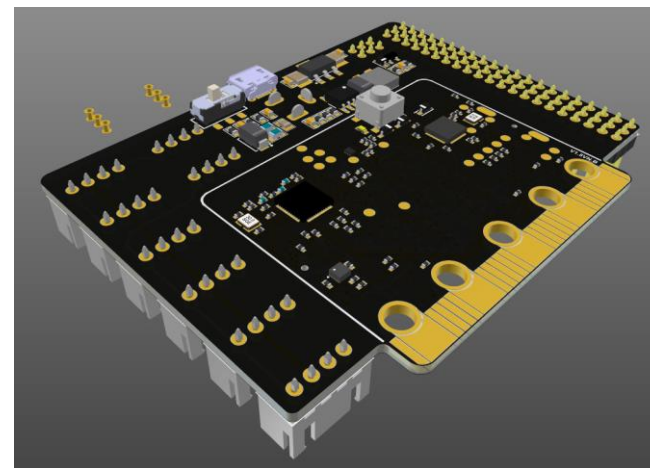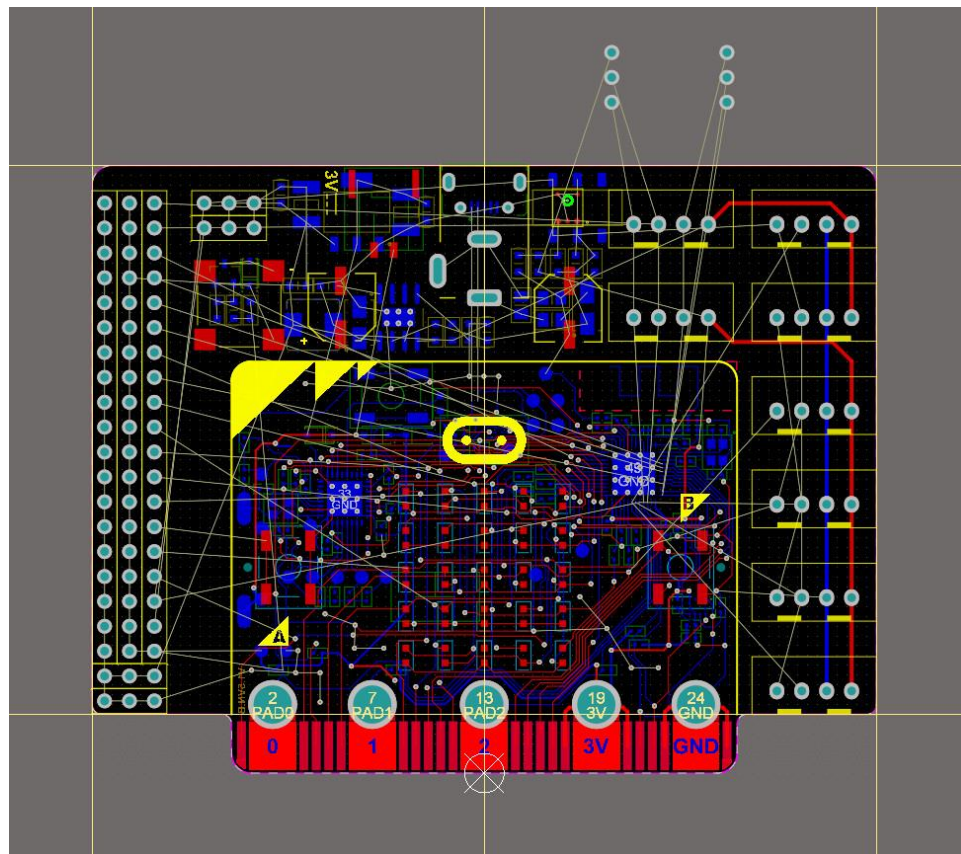


<https://ubc.sgp1.cdn.digitaloceanspaces.com/Altium/Altium%20Designer%2020.1.11%20Build%2020218.zip>

Basic Electronic Circuit Components

- Wires, Cables, and Connectors
- Batteries
- Switches
- Resistors
- LED (Light Emitted Diode)
- Exercises
- *Pull up and Pull down resistors*

Solid Core Wires

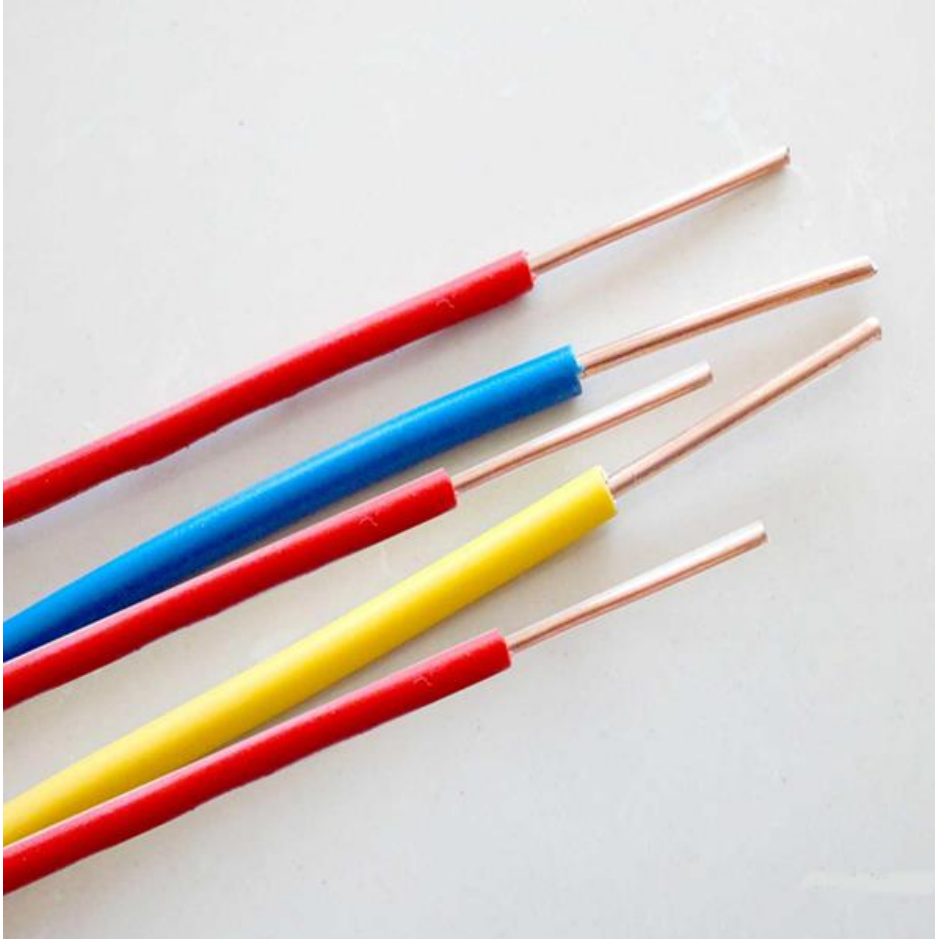

- Strong
- High current



Solid Core Applications




alamy stock photo

F66WEP
www.alamy.com

Stranded Wires (Multicore Wires)



- Soft
- Smaller current
- Easy to Draw

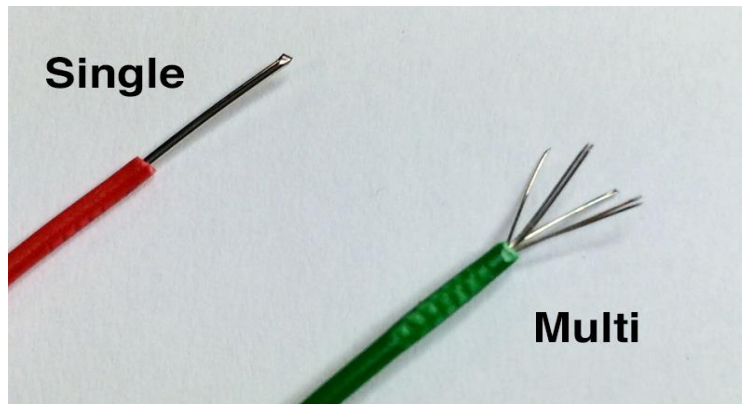

Braided Wires




- Soft and High current




Coaxial Cables


Coaxial cable

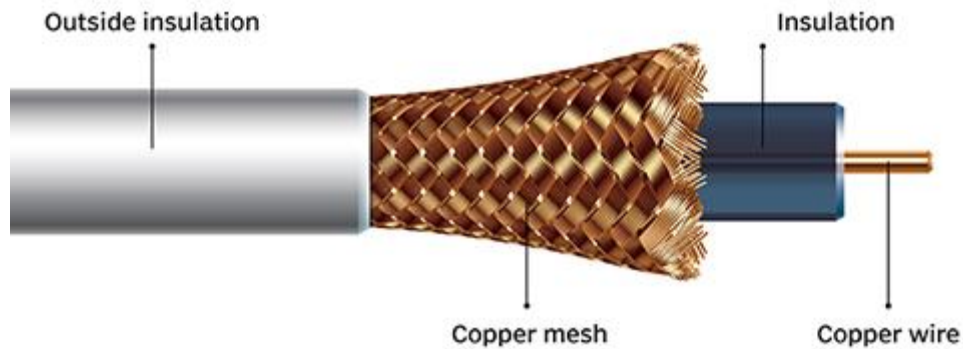

- High speed communication systems

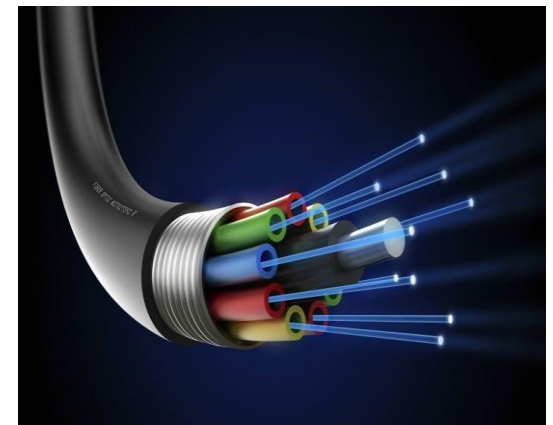

Twisted Pair Cables

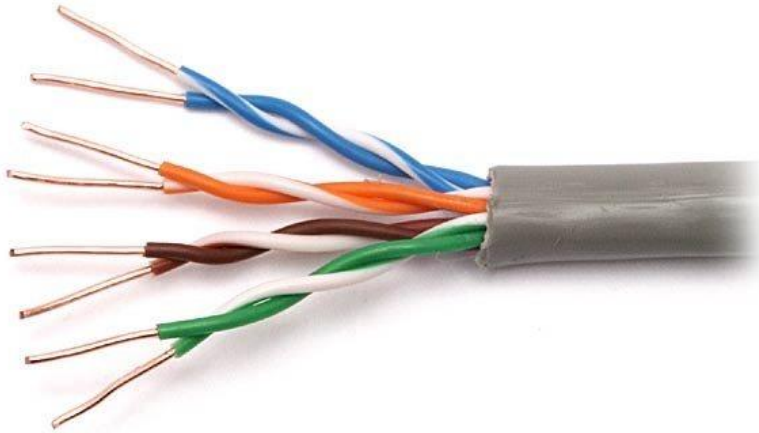

- Pulse noise avoidance
- ADSL Modem (RJ45)



Battery

- The most popular storage device



Rechargeable Batteries




- Battery capacity: 3500mAh

Super Capacitors



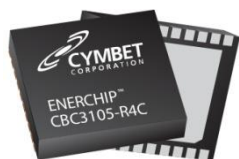Rechargeable Batteries vs Super Capacitor



[Cymbet]

500 recharge cycles

Difficult to estimate the state of charge

Low leakage current




[CapXX]

500 000 recharge cycles

Easy to estimate the state of charge

High leakage current

New Generation of Batteries

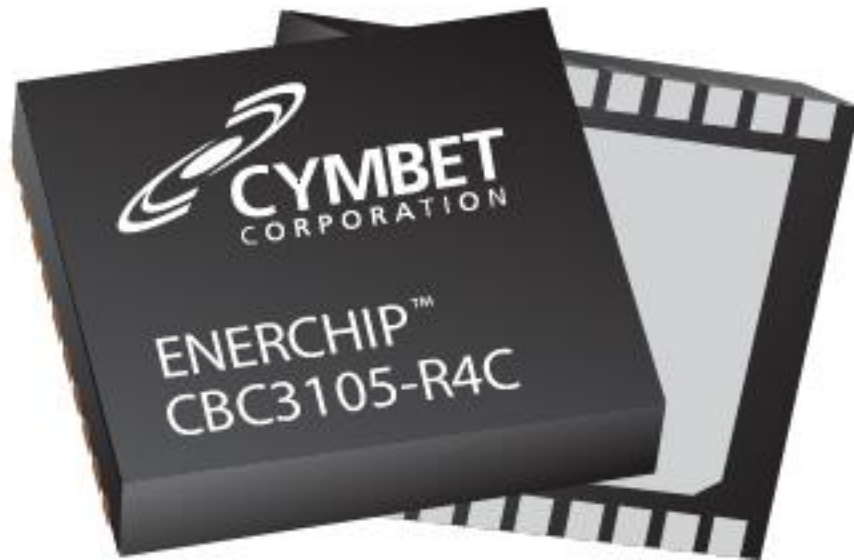

- IC Rechargeable Batteries
- Hybrid Batteries (Batteries + Capacitors)

Switch




- A switch is a mechanical device that interrupts or diverts electric current flow within a circuit

Switch Applications (1)

- Here's a simple home security alarm that's triggered into action (buzzer and light go on) when one of the normally open switches is closed. Magnetic reed switches work particularly well in such applications.


Simple Security Alarm

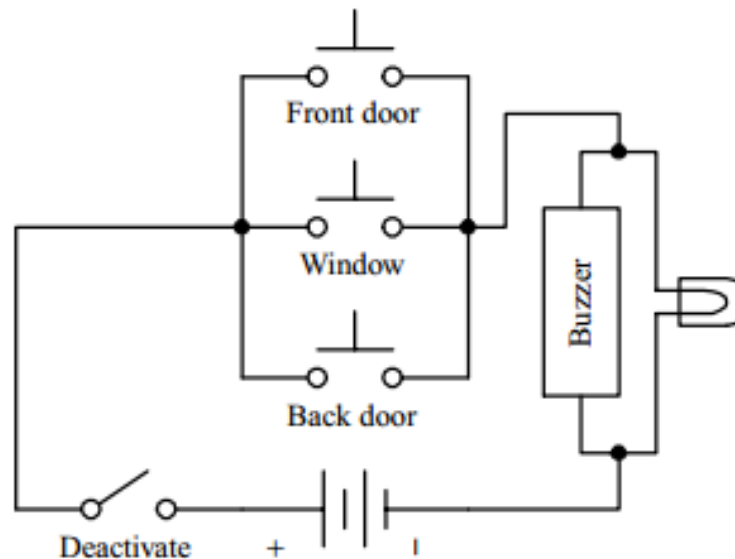

Switch Applications (2)

- Here's a switch network that allows an individual to turn a light on or off from either of two locations. This setup is frequently used in household wiring applications.


Dual-Location On/Off Switching Network

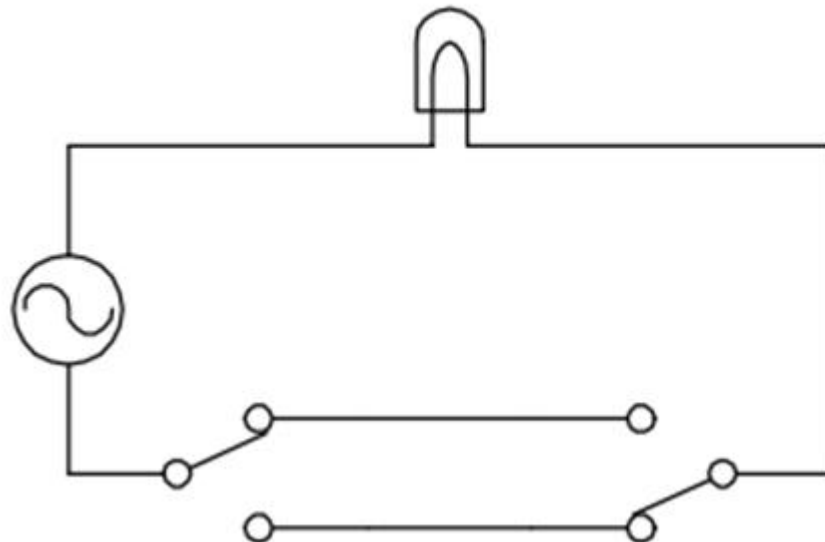

Switch Application (3)


- A DPDT switch, shown here, can be used to reverse the direction of current flow. When the switch is thrown up, current will flow through the left light-emitting diode (LED). When the switch is thrown down, current will flow through the right LED. (LEDs only allow current to flow in one direction.)

Current-Flow Reversal

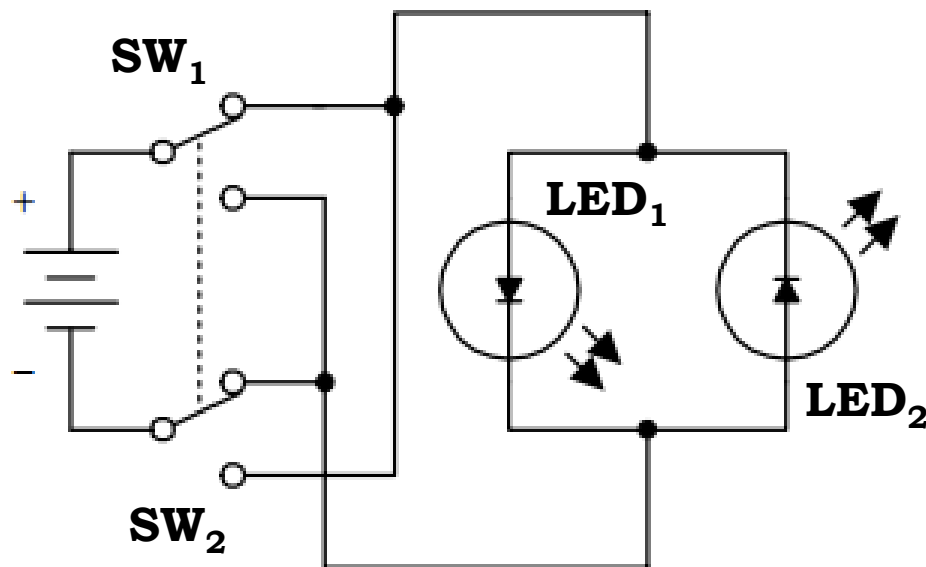


Resistors

- Resistors are electrical devices that act to reduce current flow and at the same time act to lower voltage levels within circuits.
 - The relationship between the voltage applied across a resistor and the current through it is given by $V = IR$.
- Resistors may have fixed resistances, or they may be designed to have variable resistances. They also may have resistances that change with light or heat exposure (e.g., photo-resistors, thermistors).

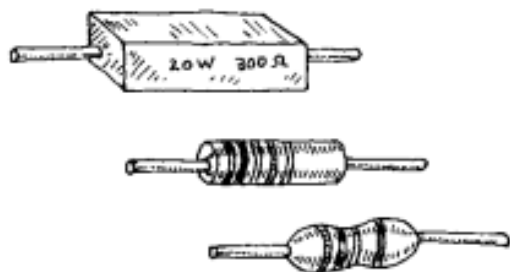

Fixed Resistors

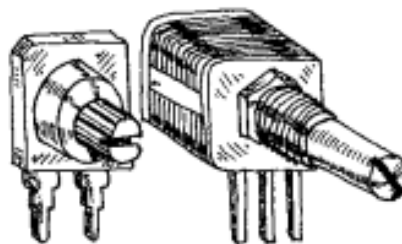


Potentiometers
and
Trimmers




Thermistors
and
Phototransistors

Resistors


Current Limiter

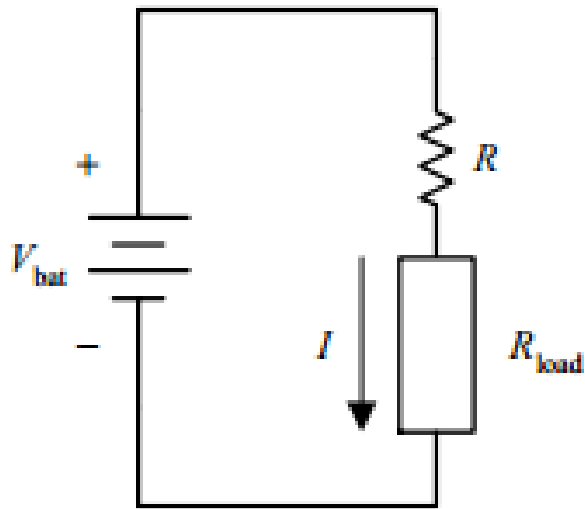


Voltage Divider

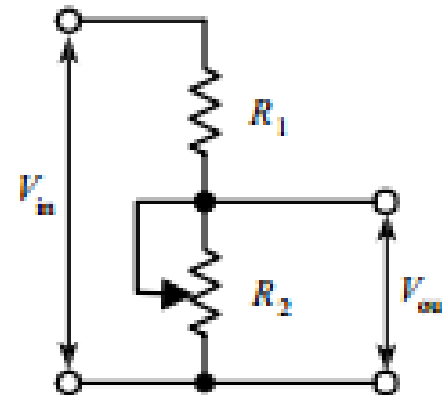


Understanding Resistor Labels

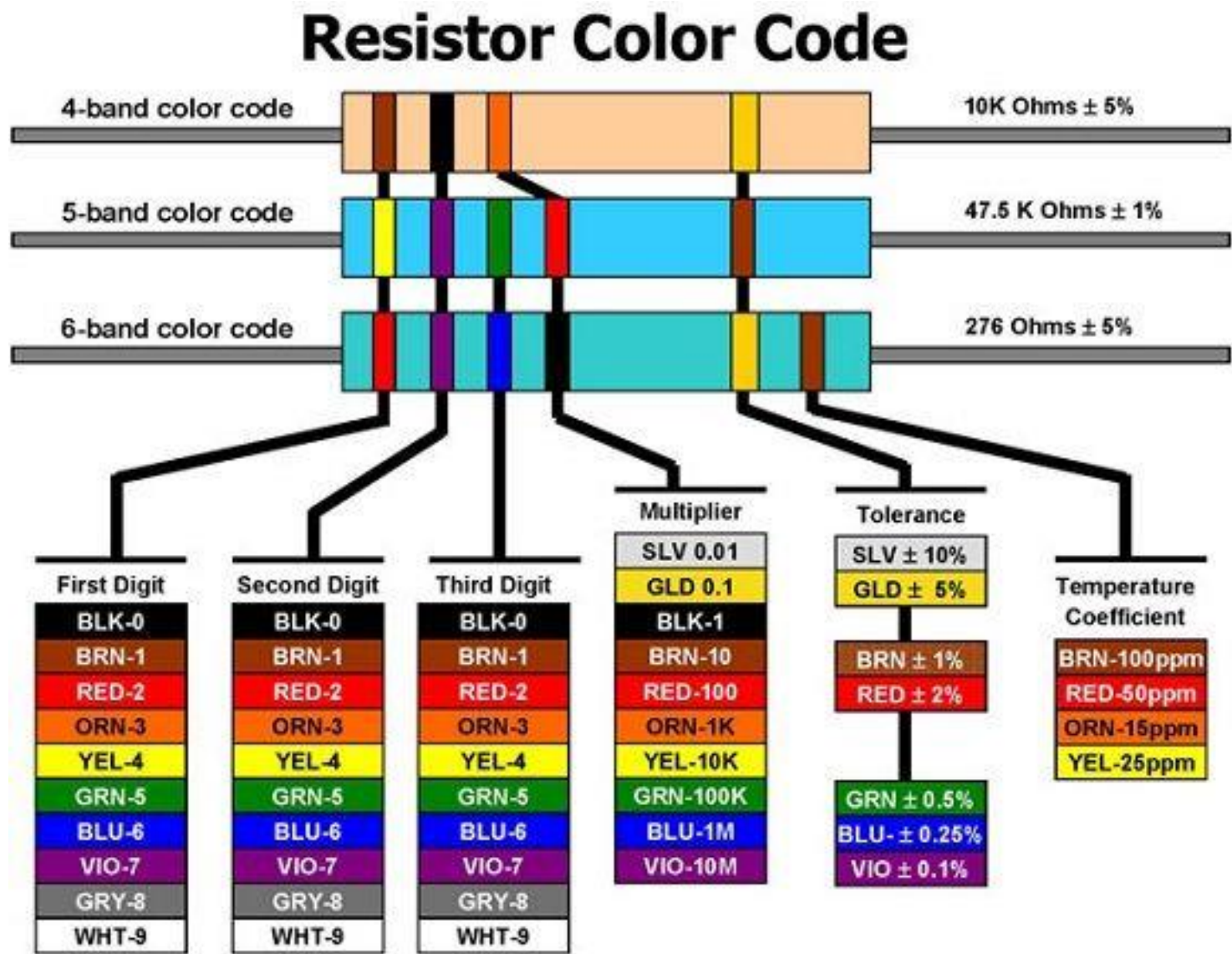


Examples

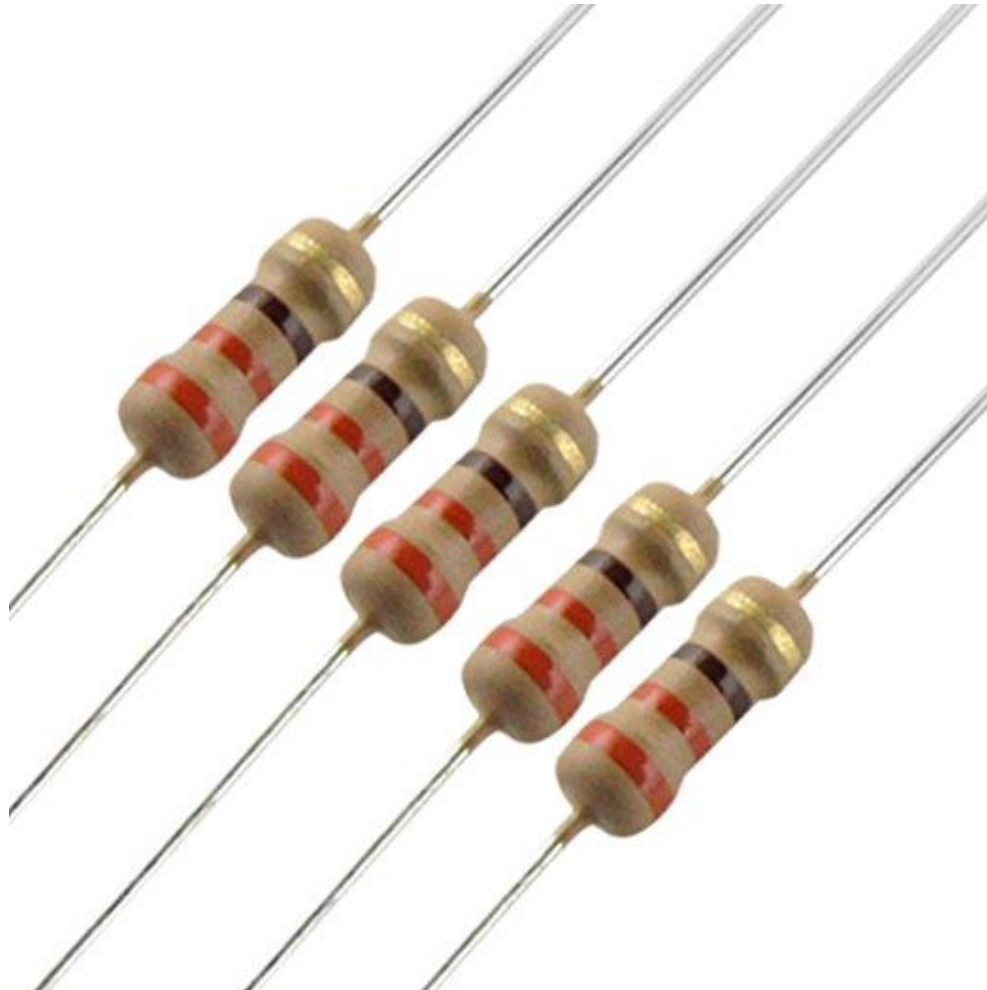

Examples

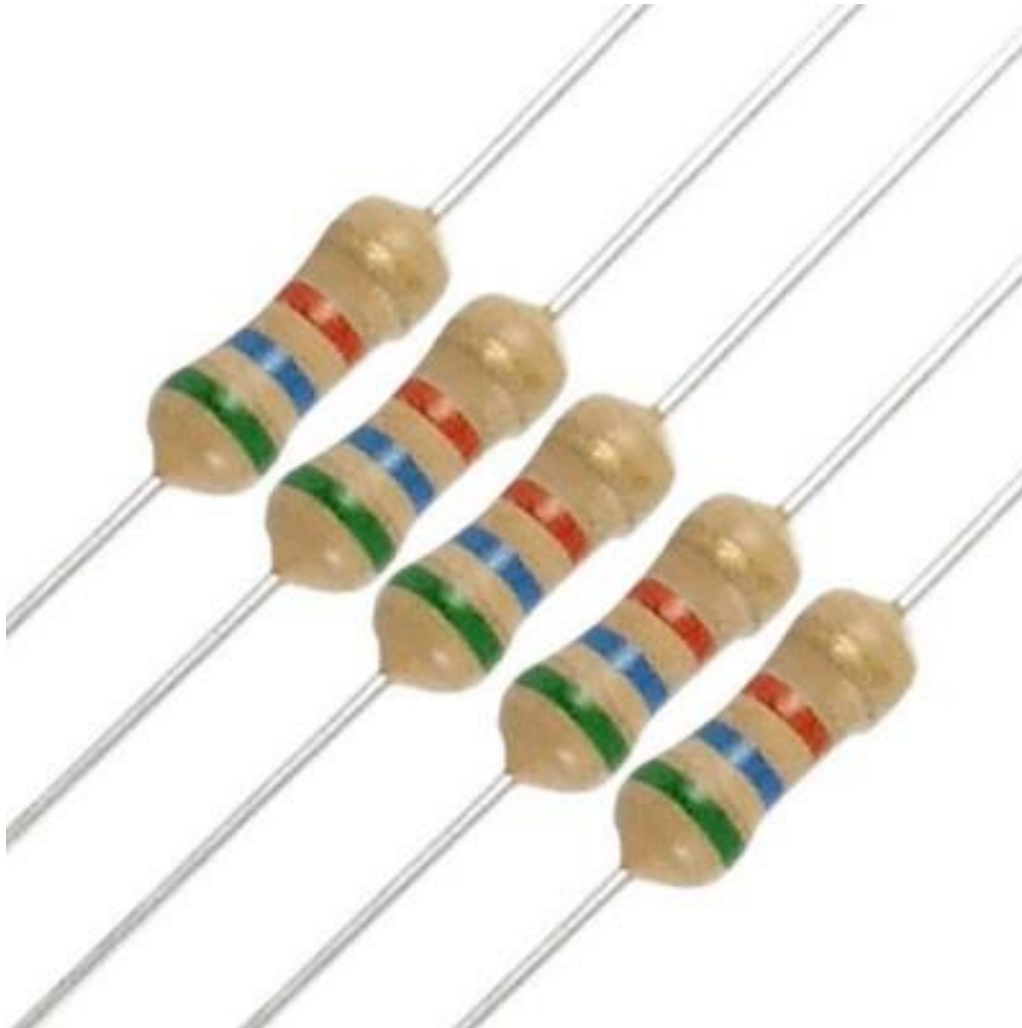


Examples

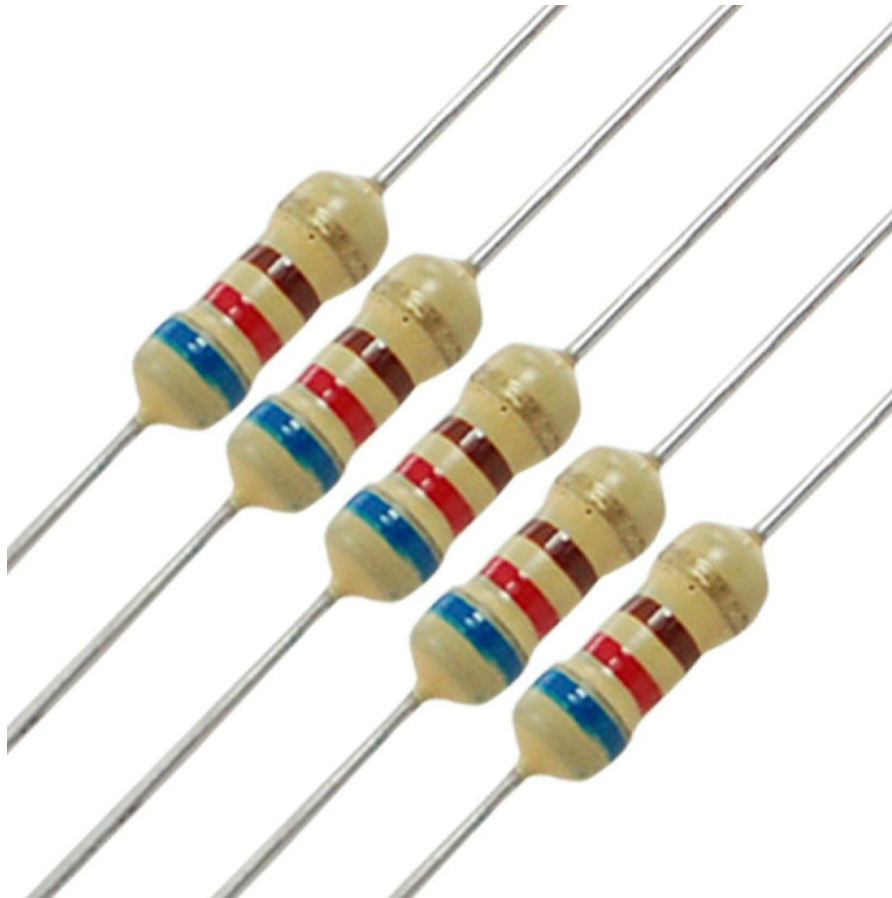

Variable Resistors

- Special kinds of variable resistors include
 - Potentiometers;
 - Rheostats; and
 - Trimmers.
- Potentiometers and rheostats are essentially the same thing, but **rheostats are used specifically for high-power ac electricity**, whereas **potentiometers typically are used with lower-level dc electricity**. Both potentiometers and rheostats are designed for **frequent adjustment**.
- Trimmers, on the other hand, are miniature potentiometers that are adjusted infrequently and usually come with pins that can be inserted into printed-circuit boards.

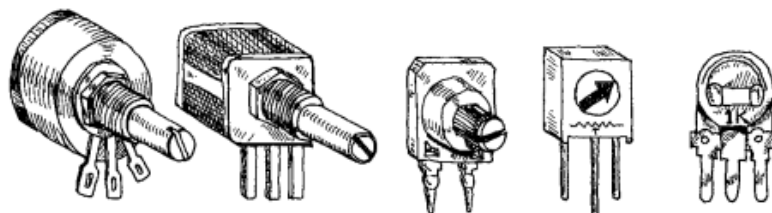

Potentiometers

Trimmers



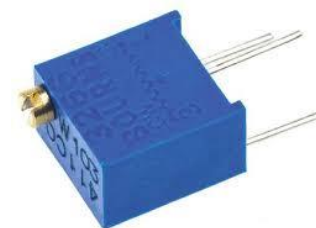
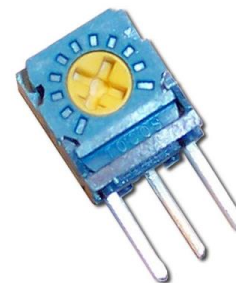
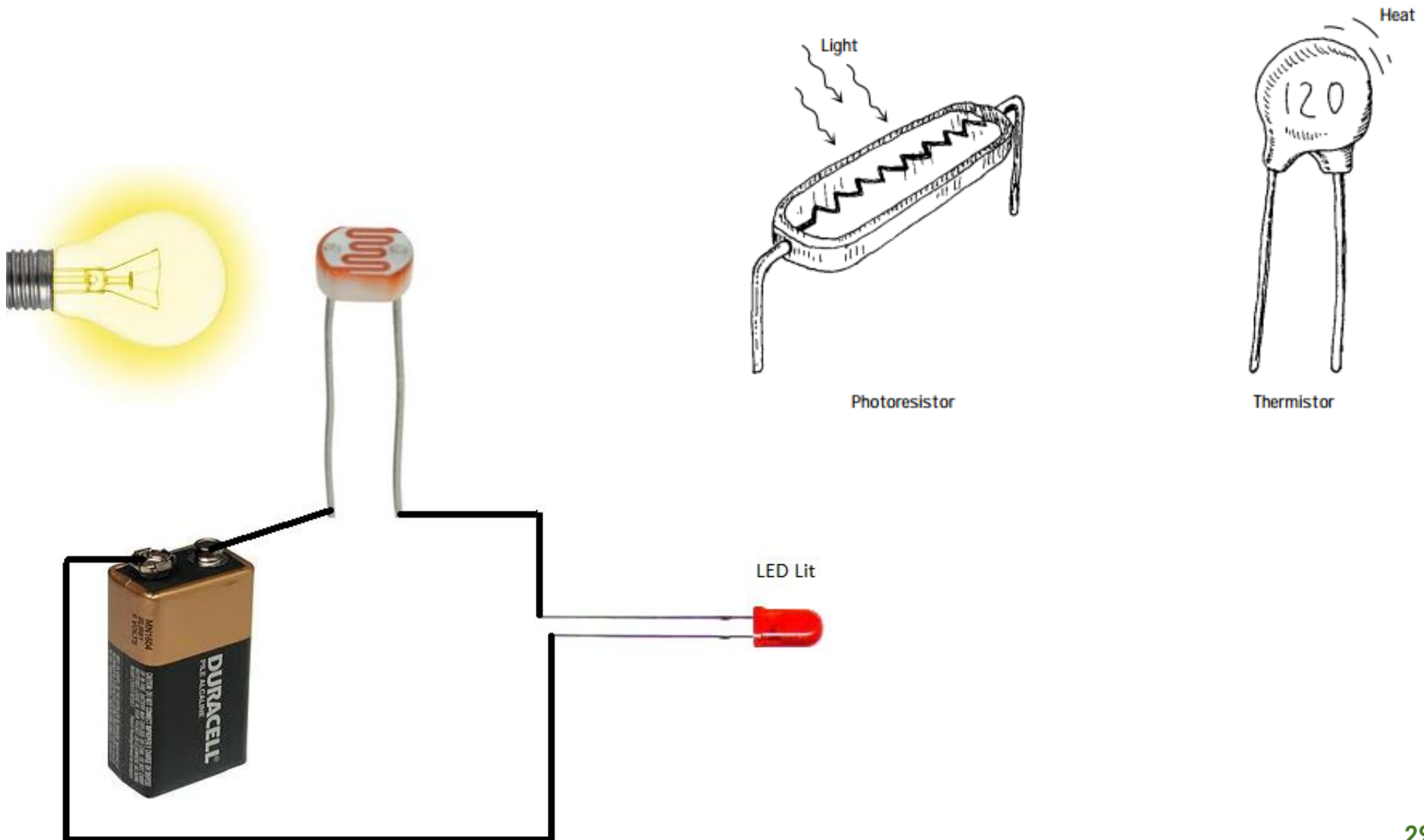
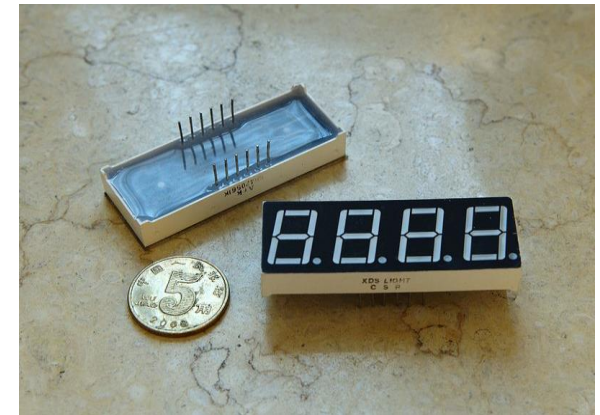




Photo-Resistors and Thermistors

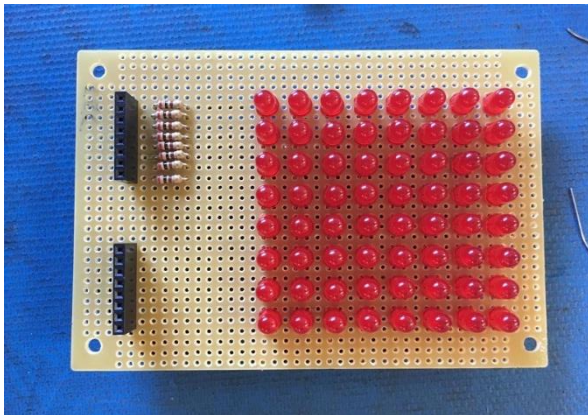


Light Emitted Diode (LED)

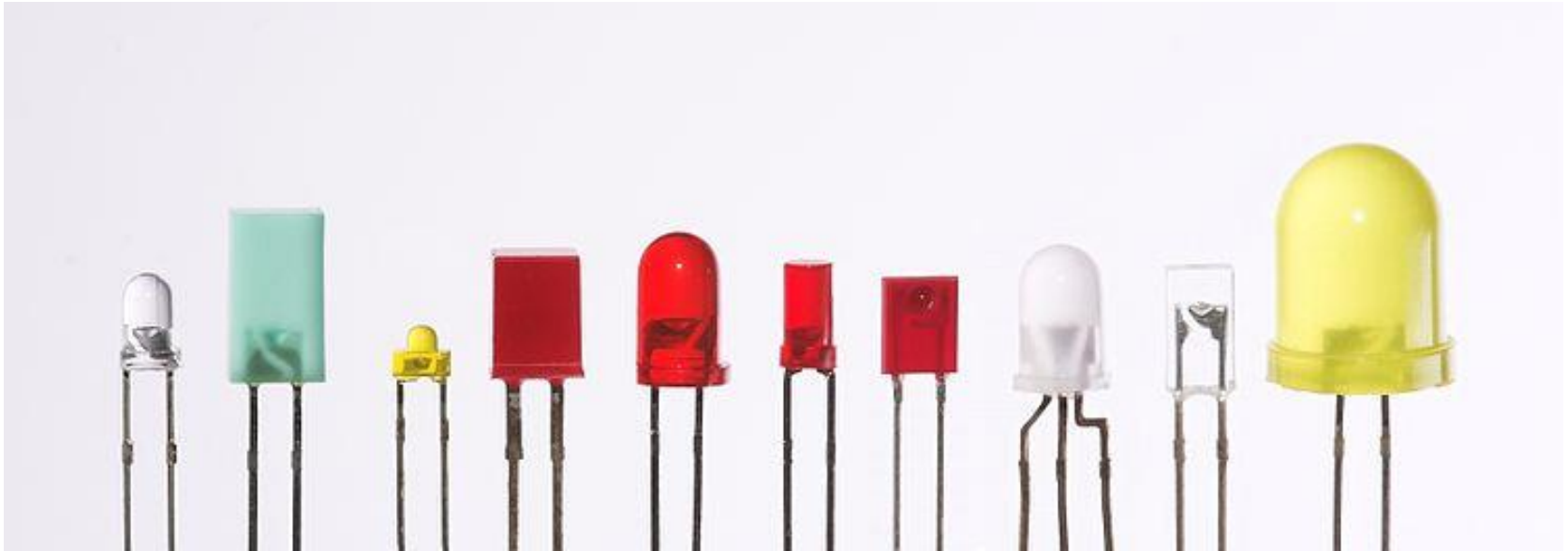

Optical Touch LED Matrix

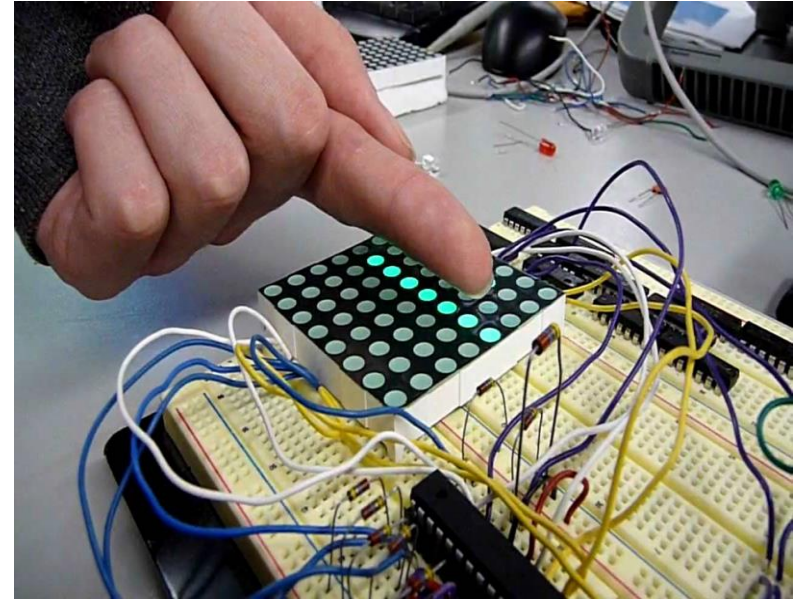
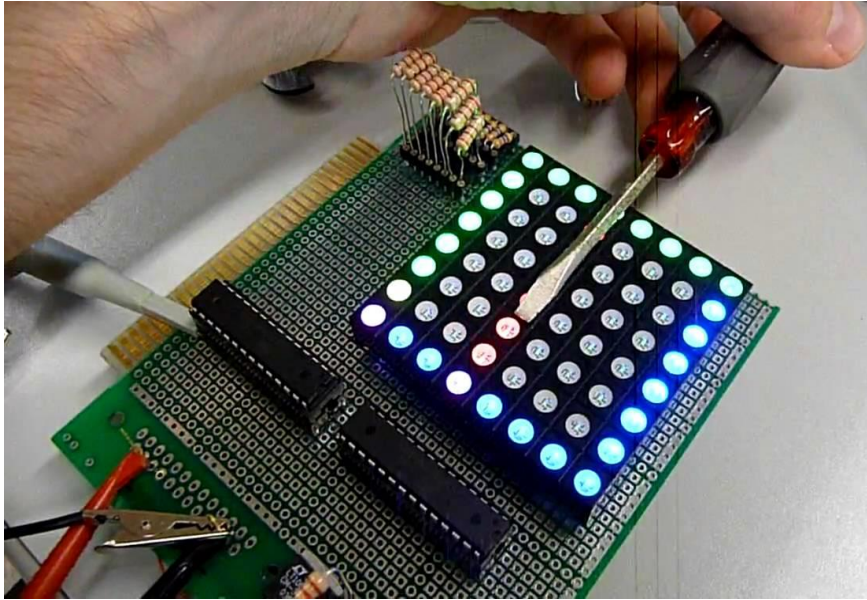


LED and Resistor Calculation

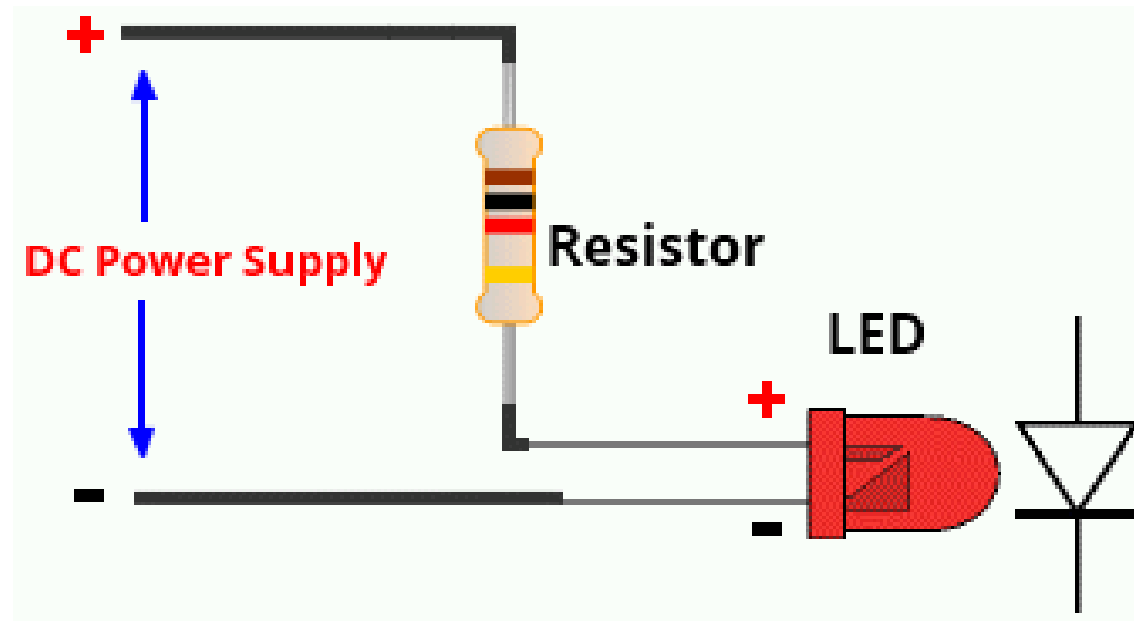

$$R = \frac{(V_s - V_{LED})}{I_{LED}}$$

LED and Resistor Calculation

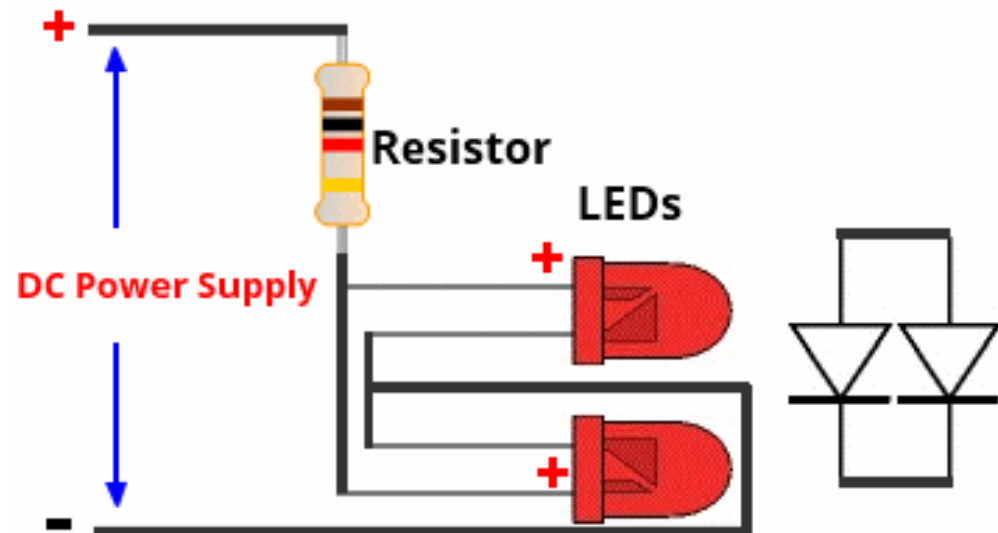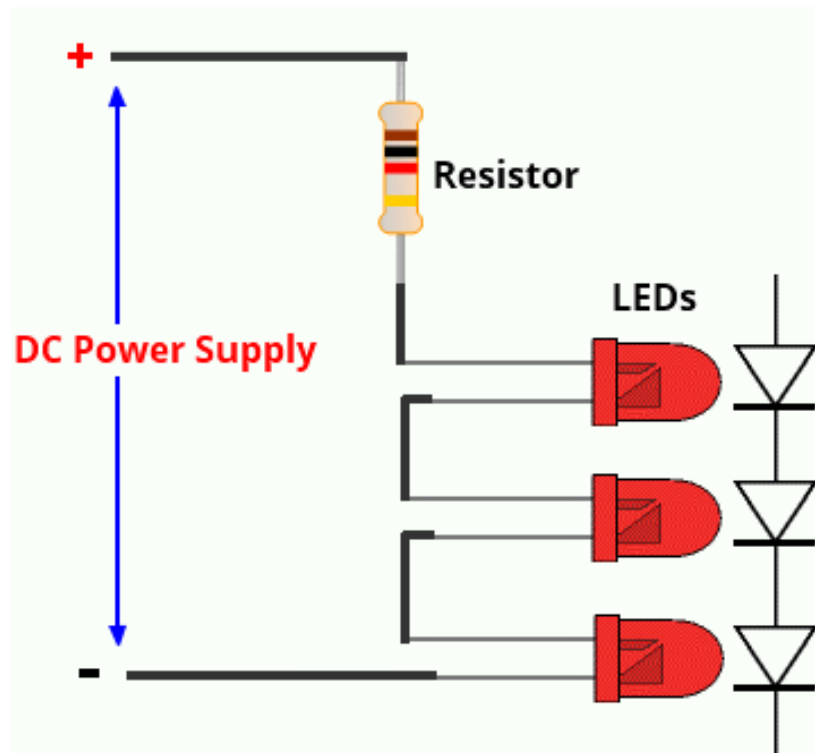


LED Applications





Exercise 1

- Analyze the circuit

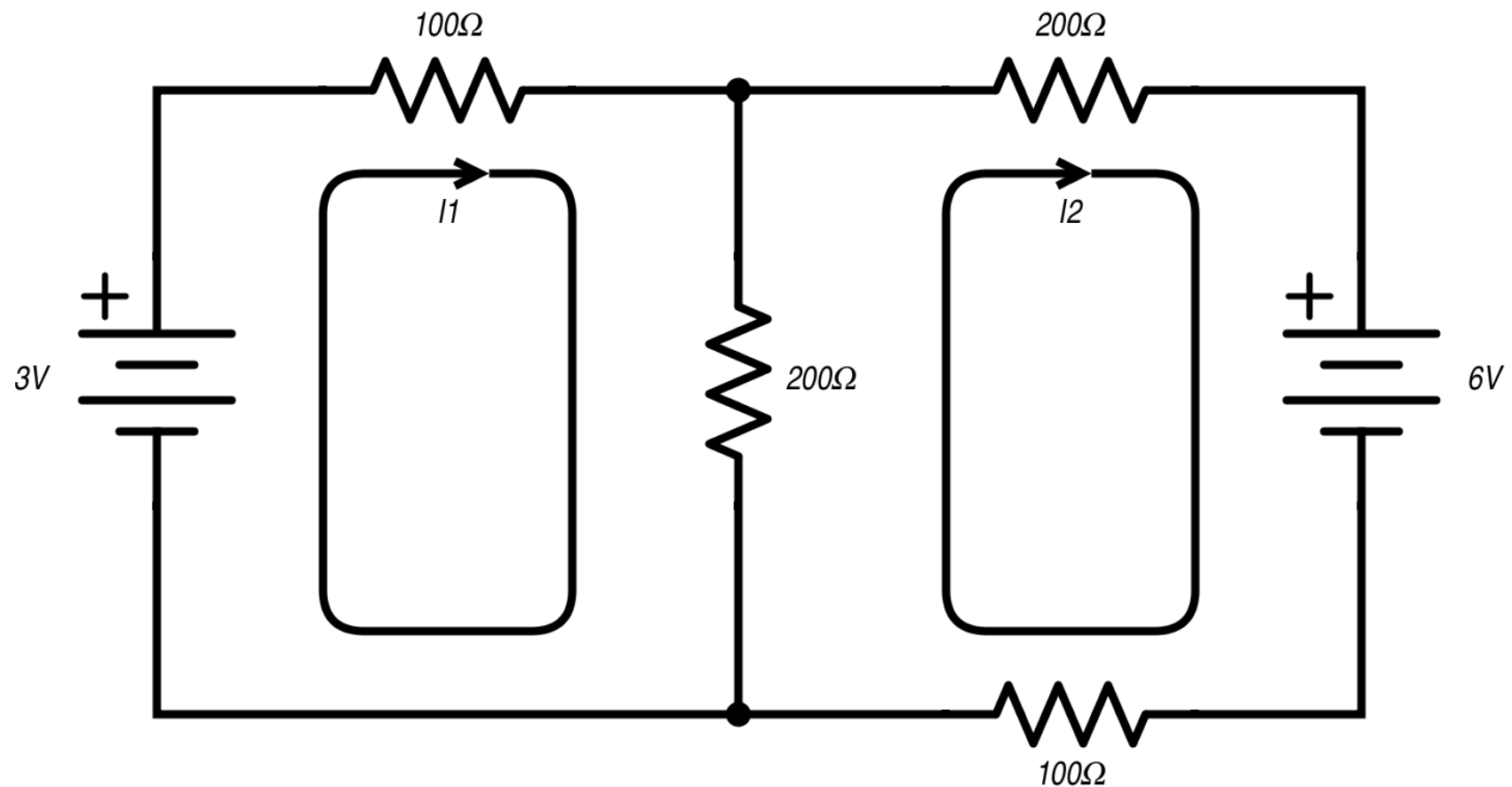



Exercise 2

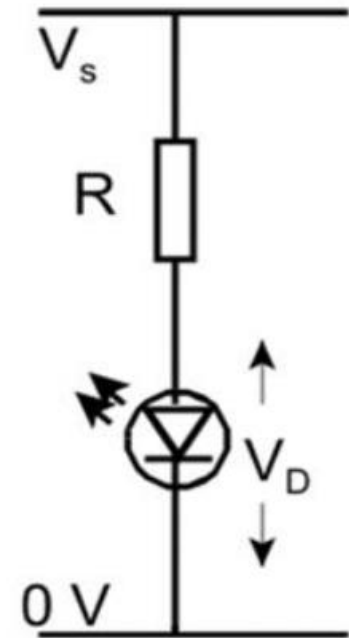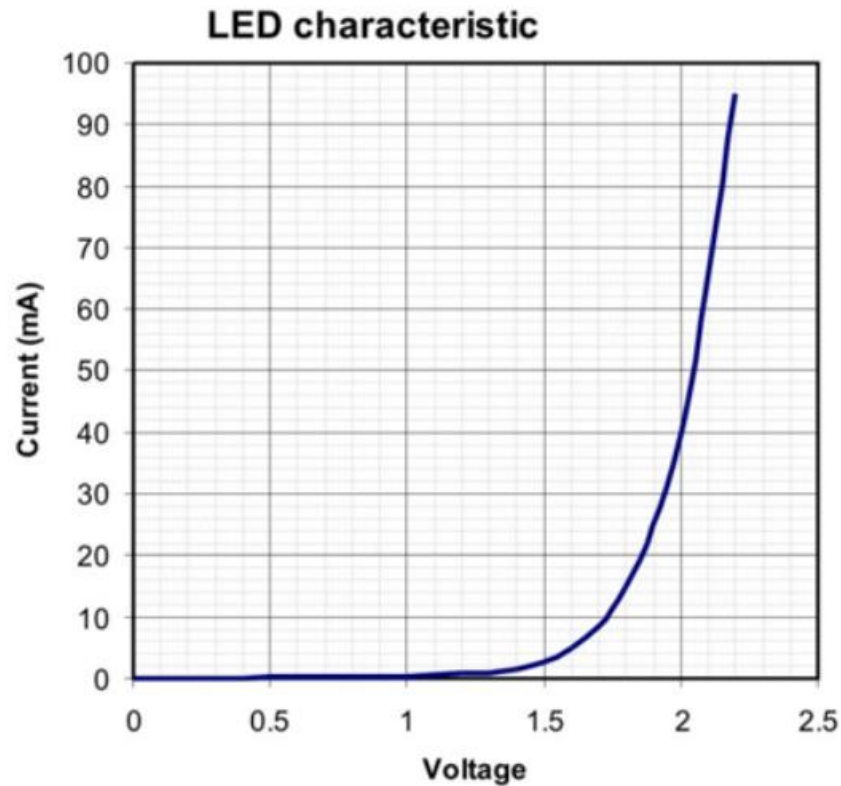

- An LED which has the characteristics shown in this graph is to be used in the circuit below in which both V_S and R can be varied. For this LED the switch on voltage (V_D) is 1.7 volt which produces a current of 10 mA at which point the LED will just glow dimly. Let us say that the LED operates brightly at 40 mA, but will fail if the current exceeds 90 mA for too long.
- Initially the power supply is set at $V_S = 6V$. What value is required for the resistor so that the LED operates at 40 mA?
- If a current of 20 mA is flowing and the resistor is 200 Ohm, what is the supply voltage?
- Find the minimum value of the resistor that could be used without damaging the LED


Pull Up and Pull Down Resistor

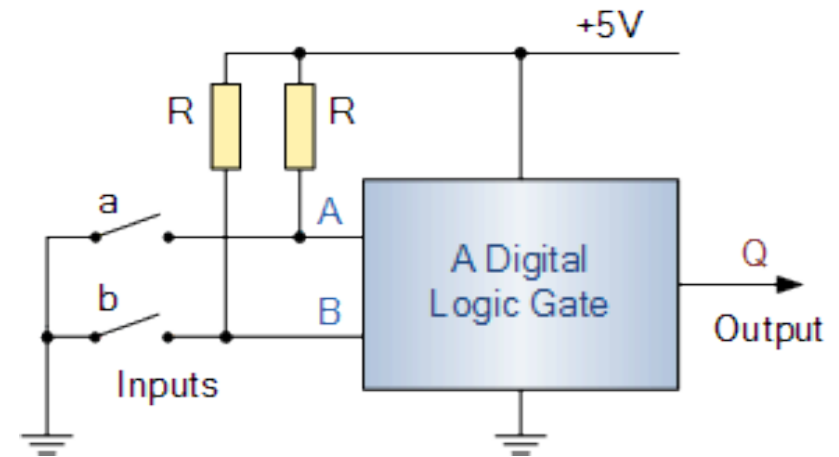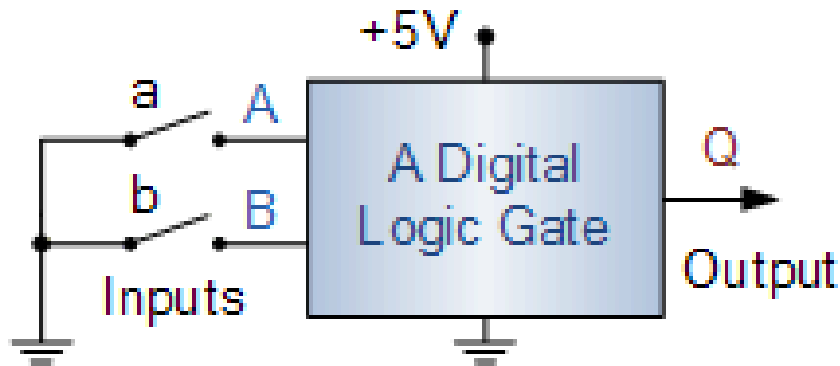- Pull-up and Pull-down resistors are used to correctly bias the inputs of digital gates to **prevent them from floating** about randomly when there is no input condition




Pull-up Resistors


- Short circuit

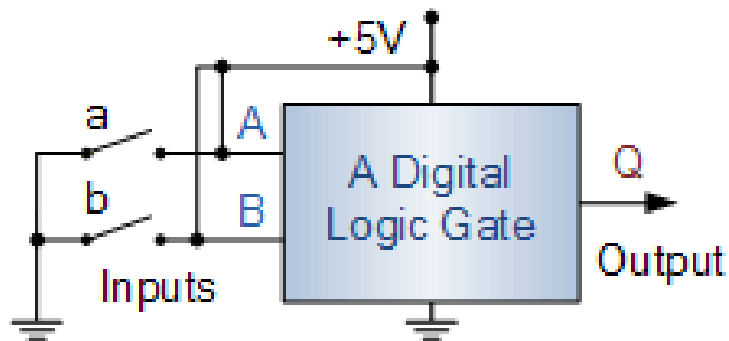

- Good connection

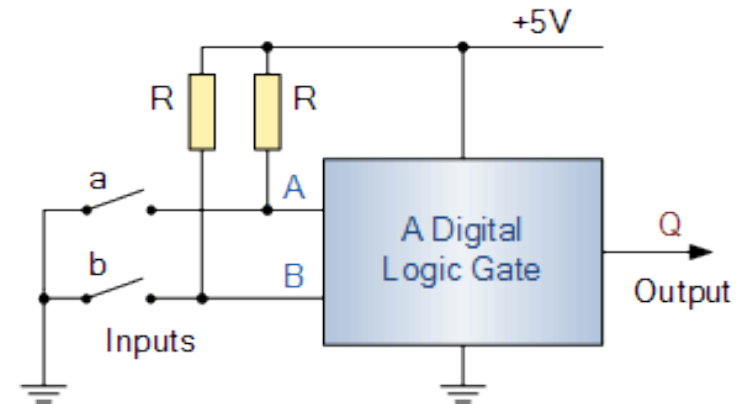

Calculating Pull-Up Resistor Value

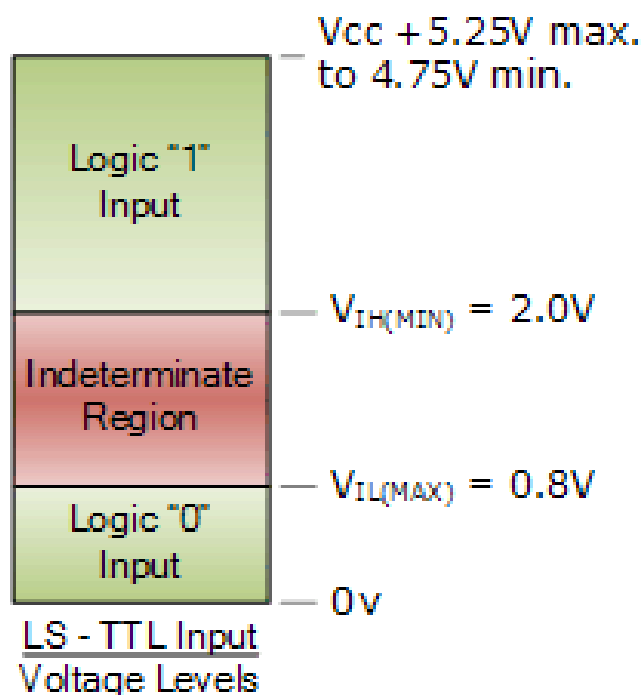

■ TTL 74LSxxx series:

- Input high: $V_{IH(min)} = 2.0V$, $I_{IH} = 20\mu A$
- Input low: $V_{IL(max)} = 0.8V$, $I_{IL} = 0.4mA$

Single Gate Pull-up Resistor Value

$$R_{MAX} = \frac{V_{CC} - V_{IH(MIN)}}{I_{IH}} = \frac{5 - 2}{20 \times 10^{-6}} = 150K\Omega$$

Multiple Gate Pull-up Resistor Value (10 inputs)

$$R_{MAX} = \frac{V_{CC} - V_{IH(MIN)}}{10 \times I_{IH}} = \frac{5 - 2}{10 \times 20 \times 10^{-6}} = 15K\Omega$$

Calculating Pull-Up Resistor Value

- A *Pull-down resistor* works in the same way as the previous pull-up resistor, except this time the logic gates input is tied to ground, logic level “0” (LOW)


$$R_{MAX} = \frac{V_{IL(MAX)} - 0}{I_{IL}} = \frac{0.8 - 0}{400 \times 10^{-6}} = 2K\Omega$$

Example

- TTL 74LS00 NAND Gates along with a single-pole double-throw switch are to be used to make a simple set-reset bistable circuit signal. Calculate: 1). The maximum pull-up resistor values if the voltage representing a logic HIGH input is to be held at 4.5 volts when the switch is open, and 2). The current flowing through the resistor when the switch is closed (assume zero contact resistance). Also draw the circuit.
- Data given: $V_{cc} = 5V$, $V_{IH} = 4.5V$, and $I_{IH(max)} = 20\mu A$

Answer

Set-Reset Bistable Circuit

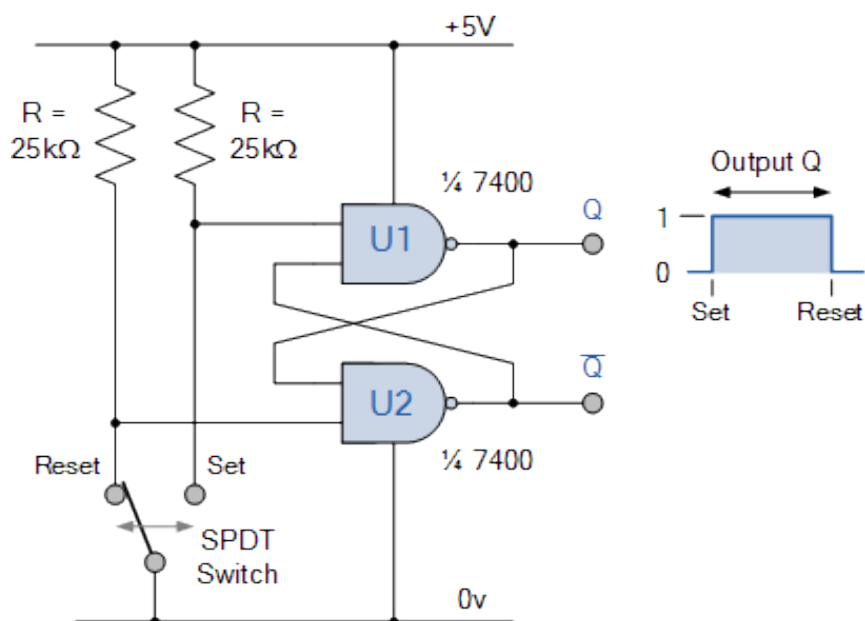

$$R_{MAX} = \frac{V_{CC} - V_{IH}}{I_{IH}} = \frac{5 - 4.5}{20 \times 10^{-6}} = 25K\Omega$$

$$I_R = \frac{V_{CC}}{R} = \frac{5V}{25k\Omega} = 200\mu A \text{ or } 0.2mA$$

Programming Arduino

Syntax

```
pinMode(pin, mode)
```

Parameters

pin: the Arduino pin number to set the mode of.

mode: INPUT, OUTPUT, or INPUT_PULLUP. See the [Digital Pins](#) page for a more complete description of the functionality.

Returns


Nothing

Example Code

The code makes the digital pin 13 OUTPUT and Toggles it HIGH and LOW


```
void setup() {  
  pinMode(13, OUTPUT);    // sets the digital pin 13 as output  
}
```


Programming on BBC Microbit

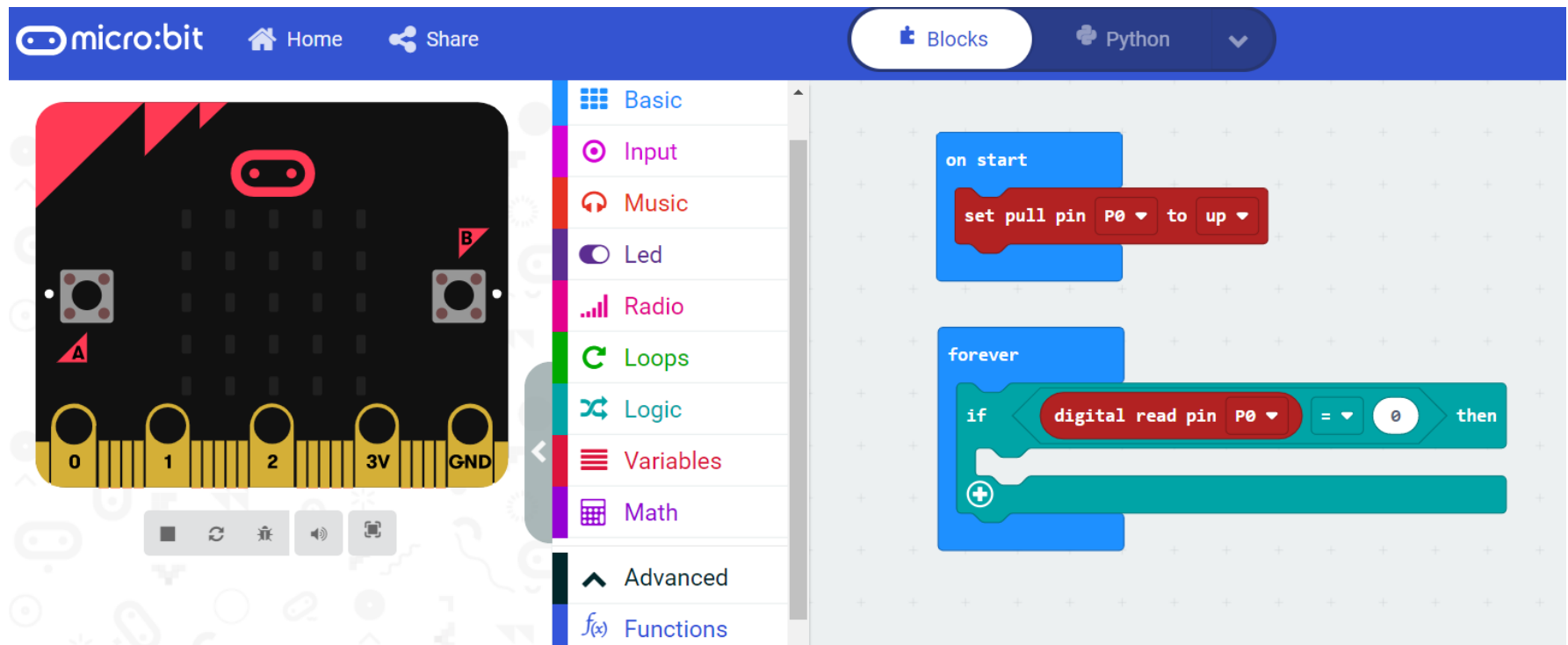

Lab Manual

- Take randomly 10 resistor pictures
- Determine the resistance based on its colors

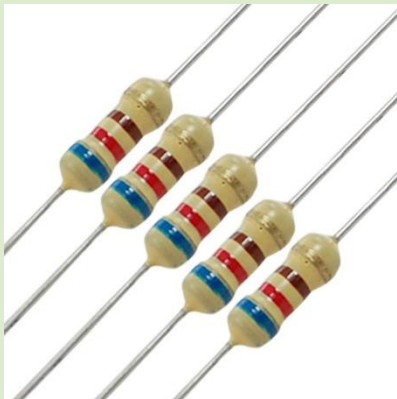No	Picture	Value
1		6200hm

Circuit Simulation on TINA TI

- TINA-TI setup file:

<http://cse.hcmut.edu.vn/vtphuong/EDAC/Tina90-TIen.exe>

- Quick manual

- https://www.youtube.com/watch?v=u7_RP1f82oo

Arduino Programming

- Student can simulate at <https://www.tinkercad.com/>

